

**POWER FACTOR
OF
ELECTRICAL SYSTEM**

BY

ELECTRICAL ENGINEER

SARDAR SABIR SALIH

DEDICATION

TO

**THOSE WHO ENLIGHTENED THE WAY
BEFORE US**

TO

**THOSE WHO ARE WAITING FOR US
TO ENLIGHTEN THE WAY FOR THEM**

TO

OUR PARENTS AND FAMILY

FOR

**OUR BELOVED COUNTRY TO LOVE
US AS MUCH AS WE LOVE IT**

**ELECTRICAL ENGINEER
SARDAR SABIR SALIH**

Power factor of electrical system

- **What is "Power Factor"?**
- **Linear circuits and Non linear circuits**
- **Definition and calculation**
- **Power factor correction of linear loads and Non-linear loads**
- **Non-sinusoidal components**
- **Switched-mode power supplies**
- **Power factor correction in non-linear loads**
- **Importance of power factor in distribution systems**
- **Measuring power factor**
- **Power factor consideration in Kurdistan**


Power factor of electrical system

What is "Power Factor"?

Power factor is a measure of how efficiently, or inefficiently, that electrical power is used by a customer, as of an AC electric power system it is defined as the ratio of the real power flowing to the load to the apparent power in the circuit, and is a dimensionless number between 0 and 1. Real power is the capacity of the circuit for performing work in a particular time. Apparent power is the product of the current and voltage of the circuit. Due to energy stored in the load and returned to the source, or due to a non-linear load that distorts the wave shape of the current drawn from the source, the apparent power will be greater than the real power.


In an electric power system, a load with a low power factor draws more current than a load with a high power factor for the same amount of useful power transferred. The higher currents increase the energy lost in the distribution system, and require larger wires and other equipment. Because of the costs of larger equipment and wasted energy, electrical utilities will usually charge a higher cost to industrial or commercial customers where there is a low power factor.

Linear loads with low power factor (such as induction motors) can be corrected with a passive network of capacitors or inductors. Non-linear loads, such as rectifiers, distort the current drawn from the system. In such cases, active or passive power factor correction may be used to counteract the distortion and raise the power factor. The devices for correction of the power factor may be at a central substation, spread out over a distribution system, or built into power-consuming equipment.

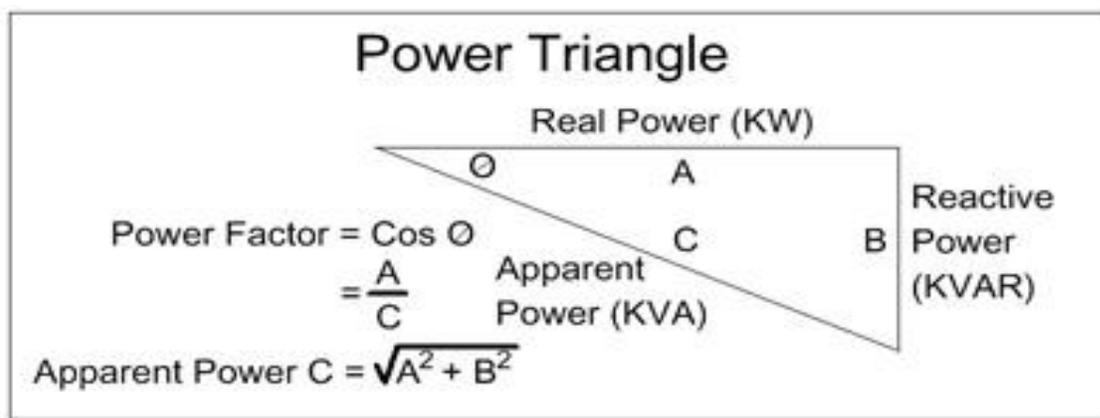


Power factor of electrical system

Linear circuits

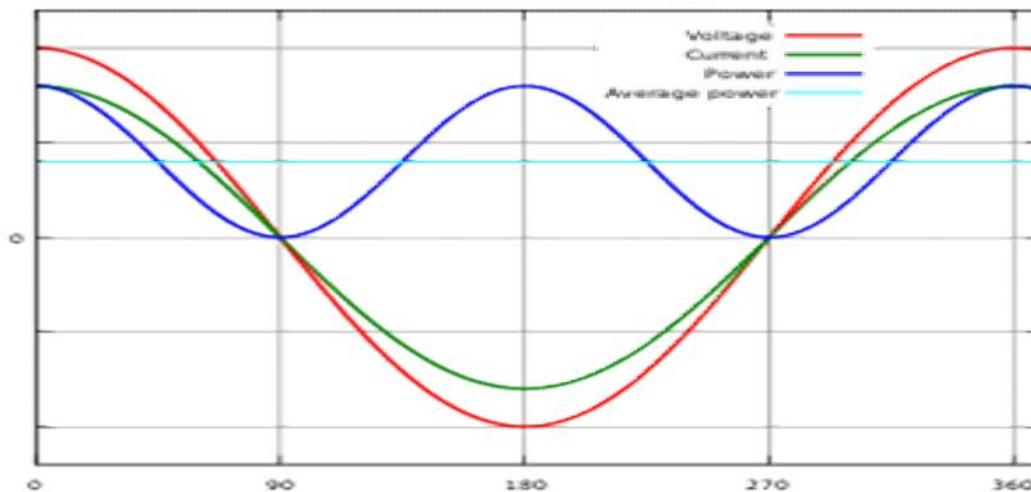


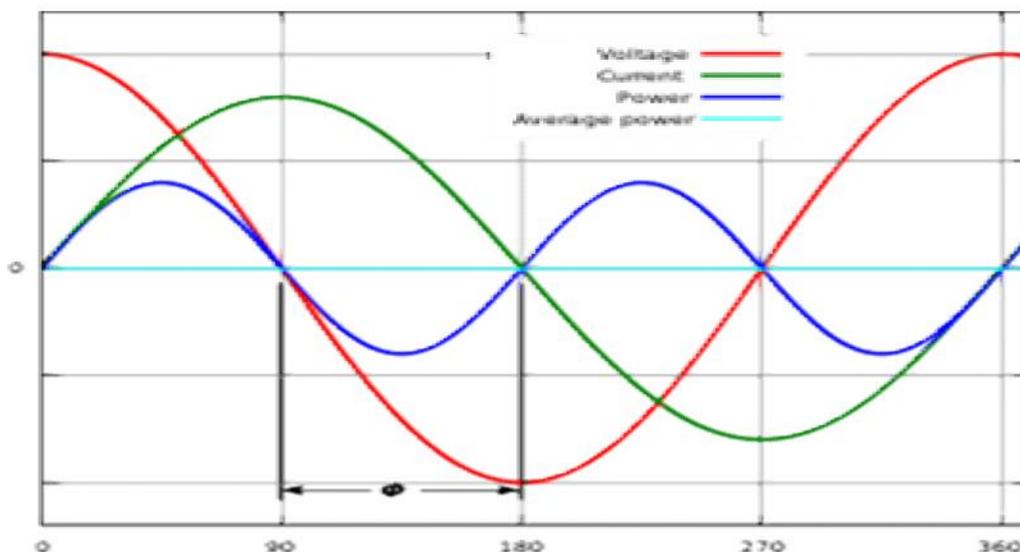Instantaneous and average power calculated from AC voltage and current with a unity power factor ($\varphi = 0$, $\cos \varphi = 1$). Since the blue line is above the axis, all power is real power consumed by the load.



Instantaneous and average power calculated from AC voltage and current with a zero power factor ($\varphi = 90$, $\cos \varphi = 0$). The blue line shows all the power is stored temporarily in the load during the first quarter cycle and returned to the grid during the second quarter cycle, so no real power is consumed.

Power factor of electrical system

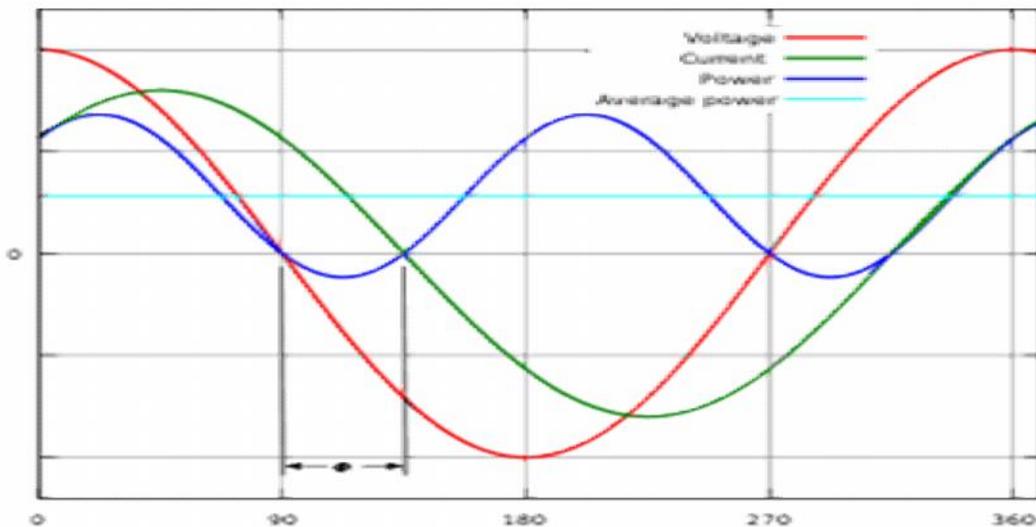

Instantaneous and average power calculated from AC voltage and current with a lagging power factor ($\varphi = 45^\circ$, $\cos \varphi = 0.71$). The blue line shows some of the power is returned to the grid during the part of the cycle labeled

In a purely resistive AC circuit, voltage and current waveforms are in step (or in phase), changing polarity at the same instant in each cycle. All the power entering the load is consumed. Where reactive loads are present, such as with capacitors or inductors, energy storage in the loads result in a time difference between the current and voltage waveforms. During each cycle of the AC voltage, extra energy, in addition to any energy consumed in the load, is temporarily stored in the load in electric or magnetic fields, and then returned to the power grid a fraction of a second later in the cycle. The "ebb and flow" of this nonproductive power increases the current in the line. Thus, a circuit with a low power factor will use higher currents to transfer a given quantity of real power than a circuit with a high power factor. A linear load does not change the shape of the waveform of the current, but may change the relative timing (phase) between voltage and current.

Circuits containing purely resistive heating elements (filament lamps, cooking stoves, etc.) have a power factor of 1.0. Circuits containing inductive or capacitive elements (electric motors, solenoid valves, lamp ballasts, and others) often have a power factor below 1.0.

Power factor of electrical system

Definition and calculation

AC power flow has the three components: real power (also known as active power) (P), measured in watts (W); apparent power (S), measured in volt-amperes (VA); and reactive power (Q), measured in reactive volt-amperes (var).

The power factor is defined as:

$$\frac{P}{S}.$$

In the case of a perfectly sinusoidal waveform, P, Q and S can be expressed as vectors that form a vector triangle such that:

$$S^2 = P^2 + Q^2.$$

If φ is the phase angle between the current and voltage, then the power factor is equal to the cosine of the angle, $|\cos \varphi|$, and:

$$|P| = |S| |\cos \varphi|.$$

Since the units are consistent, the power factor is by definition a dimensionless number between 0 and 1. When power factor is equal to 0, the energy flow is entirely reactive, and stored energy in the load returns to the source on each cycle. When the power factor is 1, all the energy supplied by the source is consumed by the load. Power factors are usually stated as "leading" or "lagging" to show the sign of the phase angle.

If a purely resistive load is connected to a power supply, current and voltage will change polarity in step, the power factor will be unity (1), and the electrical energy flows in a single direction across the network in each cycle. Inductive loads such as transformers and motors (any type of wound coil) consume reactive power with current waveform lagging the voltage. Capacitive loads such as capacitor banks or buried cable generate reactive power with current phase leading the voltage. Both types of loads will absorb energy during part of the AC cycle, which is stored in the device's magnetic or electric field, only to return this energy back to the source during the rest of the cycle.

Power factor of electrical system

For example, to get 1 kW of real power, if the power factor is unity, 1 kVA of apparent power needs to be transferred ($1 \text{ kW} \div 1 = 1 \text{ kVA}$). At low values of power factor, more apparent power needs to be transferred to get the same real power. To get 1 kW of real power at 0.2 power factor, 5 kVA of apparent power needs to be transferred ($1 \text{ kW} \div 0.2 = 5 \text{ kVA}$). This apparent power must be produced and transmitted to the load in the conventional fashion, and is subject to the usual distributed losses in the production and transmission processes.

Electrical loads consuming alternating current power consume both real power and reactive power. The vector sum of real and reactive power is the apparent power. The presence of reactive power causes the real power to be less than the apparent power, and so, the electric load has a power factor of less than 1.

Power factor correction of linear loads

A high power factor is generally desirable in a transmission system to reduce transmission losses and improve voltage regulation at the load. It is often desirable to adjust the power factor of a system to near 1.0. When reactive elements supply or absorb reactive power near the load, the apparent power is reduced. Power factor correction may be applied by an electrical power transmission utility to improve the stability and efficiency of the transmission network. Individual electrical customers who are charged by their utility for low power factor may install correction equipment to reduce those costs.

Power factor correction brings the power factor of an AC power circuit closer to 1 by supplying reactive power of opposite sign, adding capacitors or inductors that act to cancel the inductive or capacitive effects of the load, respectively. For example, the inductive effect of motor loads may be offset by locally connected capacitors. If a load had a capacitive value, inductors (also known as *reactors* in this context) are connected to correct the power factor. In the electricity industry, inductors are said to *consume* reactive power and capacitors are said to *supply* it, even though the energy is just moving back and forth on each AC cycle.

The reactive elements can create voltage fluctuations and harmonic noise when switched on or off. They will supply or sink reactive power regardless of whether there is a corresponding load operating nearby, increasing the system's no-load losses. In the worst case, reactive elements can interact with the system and with each other to create resonant conditions, resulting in system instability

Power factor of electrical system

and severe overvoltage fluctuations. As such, reactive elements cannot simply be applied without engineering analysis.

An **automatic power factor correction unit** consists of a number of capacitors that are switched by means of contactors. These contactors are controlled by a regulator that measures power factor in an electrical network. Depending on the load and power factor of the network, the power factor controller will switch the necessary blocks of capacitors in steps to make sure the power factor stays above a selected value.

Instead of using a set of switched capacitors, an unloaded synchronous motor can supply reactive power. The reactive power drawn by the synchronous motor is a function of its field excitation. This is referred to as a *synchronous condenser*. It is started and connected to the electrical network. It operates at a leading power factor and puts VARS onto the network as required to support a system's voltage or to maintain the system power factor at a specified level.

The condenser's installation and operation are identical to large electric motors. Its principal advantage is the ease with which the amount of correction can be adjusted; it behaves like an electrically variable capacitor. Unlike capacitors, the amount of reactive power supplied is proportional to voltage, not the square of voltage; this improves voltage stability on large networks. Synchronous condensers are often used in connection with high-voltage direct-current transmission projects or in large industrial plants such as steel mills.

For power factor correction of high-voltage power systems or large, fluctuating industrial loads, power electronic devices such as the Static VAR compensator or STATCOM are increasingly used. These systems are able to compensate sudden changes of power factor much more rapidly than contactor-switched capacitor banks, and being solid-state require less maintenance than synchronous condensers.



Power factor of electrical system

List below will show need of VARS to improve PF.


Individual Capacitor Rating in kVAr to improve Power Factor to 0.95 or better at all loads.

Motor Rating kW	2 Pole 3000 rpm	4 Pole 1500 rpm	6 Pole 1000 rpm
0.75	0.5 kVAr	0.5 kVAr	0.5 kVAr
1.1	0.5 kVAr	0.5 kVAr	1.0 kVAr
1.5	0.5 kVAr	1.0 kVAr	1.0 kVAr
2.2	1.0 kVAr	1.0 kVAr	1.5 kVAr
4.0	1.5 kVAr	1.5 kVAr	2.0 kVAr
5.5	2.0 kVAr	2.0 kVAr	3.0 kVAr
7.5	2.0 kVAr	2.0 kVAr	3.0 kVAr
11.0	3.0 kVAr	4.0 kVAr	5.0 kVAr
15	4.0 kVAr	5.0 kVAr	6.0 kVAr
18.5	5.0 kVAr	7.0 kVAr	8.0 kVAr
22	6.0 kVAr	8.0 kVAr	9.0 kVAr
30	8.0 kVAr	10.0 kVAr	12.0 kVAr
37	10.0 kVAr	12.0 kVAr	14.0 kVAr
45	12.0 kVAr	14.0 kVAr	16.0 kVAr
55	16.0 kVAr	22.0 kVAr	25.0 kVAr
75	18.0 kVAr	25.0 kVAr	30.0 kVAr
90	20.0 kVAr	30.0 kVAr	35.0 kVAr
110	25.0 kVAr	30.0 kVAr	40.0 kVAr
132	35.0 kVAr	40.0 kVAr	40.0 kVAr
160	40.0 kVAr	45.0 kVAr	50.0 kVAr

Power factor of electrical system

Non-linear loads

A non-linear load on a power system is typically a rectifier (such as used in a power supply), or some kind of arc discharge device such as a fluorescent lamp, electric welding machine, or arc furnace. Because current in these systems is interrupted by a switching action, the current contains frequency components that are multiples of the power system frequency. Distortion power factor is a measure of how much the harmonic distortion of a load current decreases the average power transferred to the load.

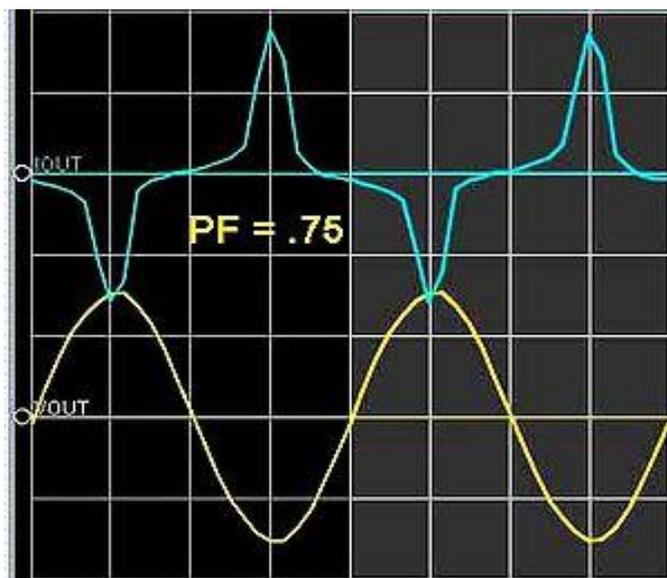

Sinusoidal voltage and non-sinusoidal current give a distortion power factor of 0.75 for this computer power supply load.

Non-sinusoidal components

Non-linear loads change the shape of the current waveform from a sine wave to some other form. Non-linear loads create harmonic currents in addition to the original (fundamental frequency) AC current. Filters consisting of linear capacitors and inductors can prevent harmonic currents from entering the supplying system.

In linear circuits having only sinusoidal currents and voltages of one frequency, the power factor arises only from the difference in phase between the current and voltage. This is "displacement power factor". The concept can be

Power factor of electrical system

generalized to a total, distortion, or true power factor where the apparent power includes all harmonic components. This is of importance in practical power systems that contain non-linear loads such as rectifiers, some forms of electric lighting, electric arc furnaces, welding equipment, switched-mode power supplies and other devices.

A typical multimeter will give incorrect results when attempting to measure the AC current drawn by a non-sinusoidal load; the instruments sense the average value of a rectified waveform. The average response is then calibrated to the effective, RMS value. An RMS sensing multimeter must be used to measure the actual RMS currents and voltages (and therefore apparent power). To measure the real power or reactive power, a watt meter designed to work properly with non-sinusoidal currents must be used.

Distortion power factor

The *distortion power factor* describes how the harmonic distortion of a load current decreases the average power transferred to the load.

The *distortion power factor* describes how the harmonic distortion of a load current decreases the average power transferred to the load.

$$\text{distortion power factor} = \frac{1}{\sqrt{1 + \text{THD}_i^2}} = \frac{I_{1, \text{rms}}}{I_{\text{rms}}}$$

THD_i is the total harmonic distortion of the load current. This definition assumes that the voltage stays undistorted (sinusoidal, without harmonics). This simplification is often a good approximation in practice. $I_{1, \text{rms}}$ is the fundamental component of the current and I_{rms} is the total current - both are root mean square-values.

The result when multiplied with the displacement power factor (DPF) is the overall, true power factor or just power factor (PF):

$$\text{PF} = \text{DPF} \frac{I_{1, \text{rms}}}{I_{\text{rms}}}$$

Power factor of electrical system

Switched-mode power supplies

Particularly important class of non-linear loads is the millions of personal computers that typically incorporate switched-mode power supplies (SMPS) with rated output power ranging from a few watts to more than 1 kW. Historically, these very-low-cost power supplies incorporated a simple full-wave rectifier that conducted only when the mains instantaneous voltage exceeded the voltage on the input capacitors. This leads to very high ratios of peak-to-average input current, which also lead to a low distortion power factor and potentially serious phase and neutral loading concerns.

A typical switched-mode power supply first makes a DC bus, using a bridge rectifier or similar circuit. The output voltage is then derived from this DC bus. The problem with this is that the rectifier is a non-linear device, so the input current is highly non-linear. That means that the input current has energy at harmonics of the frequency of the voltage.

This presents a particular problem for the power companies, because they cannot compensate for the harmonic current by adding simple capacitors or inductors, as they could for the reactive power drawn by a linear load. Many jurisdictions are beginning to legally require power factor correction for all power supplies above a certain power level.

Power factor correction in non-linear loads

Passive PFC

The simplest way to control the harmonic current is to use a filter: it is possible to design a filter that passes current only at line frequency (50 or 60 Hz). This filter reduces the harmonic current, which means that the non-linear device now looks like a linear load. At this point the power factor can be brought to near unity, using capacitors or inductors as required. This filter requires large-value high-current inductors, however, which are bulky and expensive.

A passive PFC requires an inductor larger than the inductor in an active PFC, but costs less.

Power factor of electrical system

This is a simple way of correcting the nonlinearity of a load by using capacitor banks. It is not as effective as active PFC.^{[7][8][9][10][11]} One example of this is a valley-fill circuit.

Passive PFCs are typically more power efficient than active PFCs. *Efficiency* is not to be confused with the PFC, though many computer hardware reviews conflate them.^[7] A passive PFC on a switching computer PSU has a typical power efficiency of around 96%, while an active PFC has a typical efficiency of about 94%.

Active PFC

An "active power factor corrector" (active PFC) is a power electronic system that changes the wave shape of current drawn by a load to improve the power factor. The purpose is to make the load circuitry that is power factor corrected appear purely resistive (apparent power equal to real power).^[13] In this case, the voltage and current are in phase and the reactive power consumption is zero. This enables the most efficient delivery of electrical power from the power company to the consumer

Some types of active PFC are:

- Boost
- Buck
- Buck-boost

Active power factor correctors can be single-stage or multi-stage.

In the case of a switched-mode power supply, a boost converter is inserted between the bridge rectifier and the main input capacitors. The boost converter attempts to maintain a constant DC bus voltage on its output while drawing a current that is always in phase with and at the same frequency as the line voltage. Another switch mode converter inside the power supply produces the desired output voltage from the DC bus. This approach requires additional semiconductor switches and control electronics, but permits cheaper and smaller passive components. It is frequently used in practice. For example, SMPS with passive PFC can achieve power factor of about 0.7–0.75, SMPS with active PFC, up to 0.99 power factor, while a SMPS without any power factor correction has a power factor of only about 0.55–0.65.

Power factor of electrical system



Importance of power factor in distribution systems

Power factors below 1.0 require a utility to generate more than the minimum volt-amperes necessary to supply the real power (watts). This increases generation and transmission costs. For example, if the load power factor were as low as 0.7, the apparent power would be 1.4 times the real power used by the load. Line current in the circuit would also be 1.4 times the current required at 1.0 power factor, so the losses in the circuit would be doubled (since they are proportional to the square of the current). Alternatively all components of the system such as generators, conductors, transformers, and switchgear would be increased in size (and cost) to carry the extra current.

Utilities typically charge additional costs to customers who have a power factor below some limit, which is typically 0.9 to 0.95. Engineers are often interested in the power factor of a load as one of the factors that affect the efficiency of power transmission.

Measuring power factor

Power factor in a single-phase circuit (or balanced three-phase circuit) can be measured with the wattmeter-ammeter-voltmeter method, where the power in watts is divided by the product of measured voltage and current. The power factor of a balanced poly phase circuit is the same as that of any phase. The power factor of an unbalanced poly phase circuit is not uniquely defined.

A direct reading power factor meter can be made with a moving coil meter of the electrodynamic type, carrying two perpendicular coils on the moving part of

Power factor of electrical system

the instrument. The field of the instrument is energized by the circuit current flow. The two moving coils, A and B, are connected in parallel with the circuit load. One coil, A, will be connected through a resistor and the second coil, B, through an inductor, so that the current in coil B is delayed with respect to current in A. At unity power factor, the current in A is in phase with the circuit current, and coil A provides maximum torque, driving the instrument pointer toward the 1.0 mark on the scale. At zero power factor, the current in coil B is in phase with circuit current, and coil B provides torque to drive the pointer towards 0. At intermediate values of power factor, the torques provided by the two coils add and the pointer takes up intermediate positions.

Another electromechanical instrument is the polarized-vane type. In this instrument a stationary field coil produces a rotating magnetic field, just like a polyphase motor. The field coils are connected either directly to polyphase voltage sources or to a phase-shifting reactor if a single-phase application. A second stationary field coil, perpendicular to the voltage coils, carries a current proportional to current in one phase of the circuit. The moving system of the instrument consists of two vanes that are magnetized by the current coil. In operation the moving vanes take up a physical angle equivalent to the electrical angle between the voltage source and the current source. This type of instrument can be made to register for currents in both directions, giving a four-quadrant display of power factor or phase angle.

Digital instruments can be made that either directly measure the time lag between voltage and current waveforms and so calculate the power factor, or by measuring both true and apparent power in the circuit and calculating the quotient. The first method is only accurate if voltage and current are sinusoidal; loads such as rectifiers distort the waveforms from the sinusoidal shape.



Power factor of electrical system

Power factor consideration in Kurdistan

Simply power factor improving or correction will lead for below benefits:

1. Reduction of heating losses in transformers and distribution equipment
2. Longer equipment life
3. Stabilized voltage levels
4. Increased capacity of your existing system and equipment.
5. Improved profitability.
6. Lowered expenses.

Due above reasons, recently led companies in Kurdistan and Iraq to pay attention spending on improving the power factor in their companies specially those relying mostly on power generators to cover their electric power consumption, encouraging our electrical engineers to focus also on this section helping our companies to manage their loads in engineering way.

Power Factor Correction Unit is available in Kurdistan as in figure below, all what is needed is to connect with the load by the board and adjust the PLC to keep PF for 1



Power factor of electrical system

Automatic Capacitor Bank.

1. Regulator
2. Network connection points
3. Fuses
4. Contactors
5. Capacitors (single-phase units, delta-connection)
6. Transformer 400/230 Volts for control power (contactors, ventilation,...)

